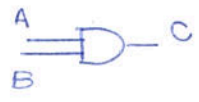


COMPUERTAS LÓGICAS (TP 6)


AND



$C = A \cdot B$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


OR

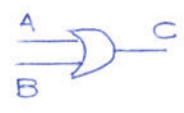

$C = A + B$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


NOT

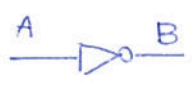

$B = \bar{A}$

A	B
0	1
1	0


NAND

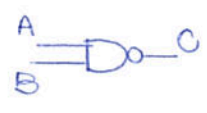

$C = \overline{A \cdot B}$

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


NOR

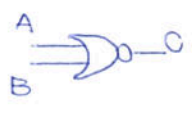

$C = \overline{A + B}$

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


OR EXCLUSIVA

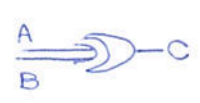

$C = A \oplus B$
 $C = (A + B) \cdot (\overline{A \cdot B})$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

NOR EXCLUSIVA

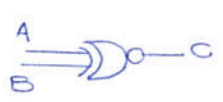

$C = \overline{A \oplus B}$

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

DISTRIBUTIVA

$A(B + C) = AB + AC$
 $A + BC = (A + B)(A + C)$

ASOCIATIVA

$A(B \cdot C) = (A \cdot B)C$
 $A + (B + C) = (A + B) + C$

ABSORCIÓN

$A + AB = A$
 $A(A + B) = A$

MORGAN

$\overline{A \cdot B} = \bar{A} \cdot \bar{B}$
 $\overline{A + B} = \bar{A} + \bar{B}$

OTRAS

$A + \bar{A}B = A + B$
 $A(\bar{A} + B) = AB$
 $A + \bar{A} = 1$
 $A \cdot \bar{A} = 0$
 $A \cdot A = A$

CIRCUITOS (TP 9)

DEDOJO SET-RESET (LATCH S-R)

S	R	Q_n
0	0	Q_{n-1}] Memoria
0	1	0] Reset
1	0	1] Set
1	1	0] No se usa → indeterminado ambiguo

\bar{S}	\bar{R}	Q_n
0	0	0] Est. ambiguo
0	1	1] Set
1	0	0] Reset
1	1	Q_{n-1}] Memoria

$E=0 \rightarrow$ Todo 0

$E=1 \rightarrow$ Depende de S y R

FUP FLOP J-K


J	K	Q_n
0	0	Q_{n-1}
0	1	0
1	0	1
1	1	\bar{Q}_{n-1}] Resuelve el prob. de incet.

FUP FLOP D

D	Q_n
0	0] Reset
1	1] Set


MAESTRO/ESCLAVO \rightarrow Flanco descendiente

CONTADORES (TP 10)

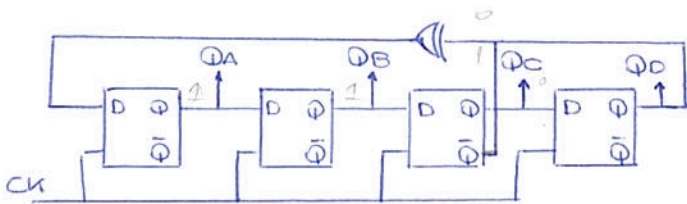


Q_A	Q_B	Q_C	Q_D
0	0	0	0 \rightarrow Estado inicial
1	0	0	0
1	1	0	0
1	1	1	0
1	0	1	1

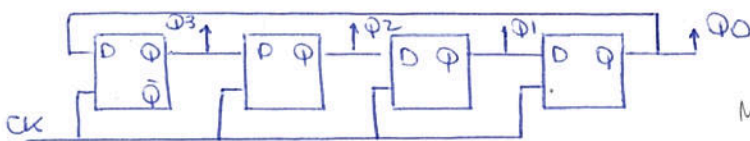CONTADOR DE ANILLO CON 4 Flip Flops TIPO D




Q_3	Q_2	Q_1	Q_0
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

Módulo 4

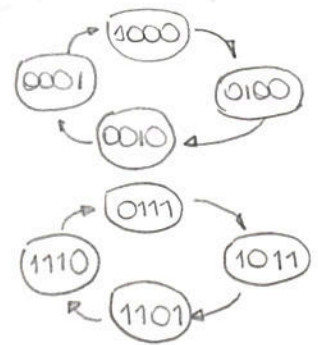


CONTADOR DE JOHNSON O DE MOBIUS

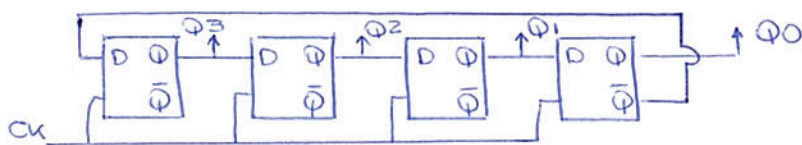

Q_3	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1

Módulo 8

TP 2: SENSORES Y ACTUADORES

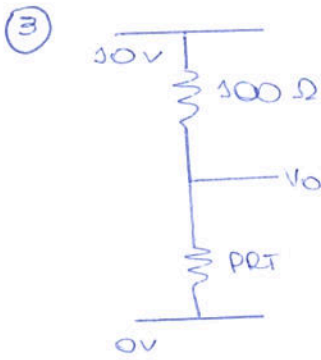

$$\Delta V = (0 - V_0) + (V_0 - 10)$$

$$V_0 = R_{PRT} \cdot i$$

$$V_0 = 100 \cdot i + 10$$

$$V_0 = 100i - 100i$$

$$R_{PRT} \cdot i = 10 - 100i$$

$$i = \frac{10}{(100 + R_{PRT})} \Rightarrow \text{No lineal}$$

$$R_{PRT} = 100 + 0,385t \rightarrow \text{del ej 2.}$$

3

TP 3: AMPLIFICACION

- 2) $a = 20 = A_v = V_0 / V_i$ ideal
 $R_e = 10 \mu\Omega$
 $R_s = 75 \text{ k}\Omega$
 $V = 1 \text{ V}$
 $R_{sv} = 200 \Omega$
 $R_{osa} = 1 \mu\Omega$



casada \rightarrow ampl. en serie

$$V_i = \frac{V \cdot R_e}{R_e + R_v} = 0,117 \text{ V}$$

$$A_v \cdot V_i \cdot \frac{R_c}{R_s + R_c} = V_0 = 0,25 \text{ V}$$

$$W_L = \frac{1}{c(R_0 + R_s)}$$

de acopl
 c. EN SERIE \rightarrow PASAN f altas; corte inferior
 c EN PARALELO \rightarrow PASAN f bajas; corte sup.

$$G_v \text{ (dB)} = 20 \log_{10} \frac{V_0}{V_i}$$

$$G_p \text{ (dB)} = 10 \log_{10} \frac{V_0}{V_i}$$

FRECUENCIA
 OCTAVA = $2^n \cdot f$
 DÉCIMA = $10^n \cdot f$

Amp. 741

- $G_T = 106 \text{ dB}$
- $R_e = 2 \text{ M}\Omega$
- $R_s = 75 \Omega$
- $i = 20 \text{ mA}$





Ej. 1 octava por encima de 10 Hz
 $= 2^1 \cdot 10 = 20 \text{ Hz}$

TP 3: AMPLIFICACIÓN

⑤ $G_{v \text{ med}} = 10 = 20 \log_{10}(10) = 20 \text{ dB}$

$F. \text{mf} = 100 \text{ Hz}$




$F. \text{Sup} = 10000 \text{ Hz}$

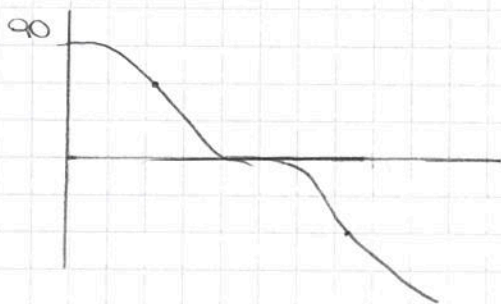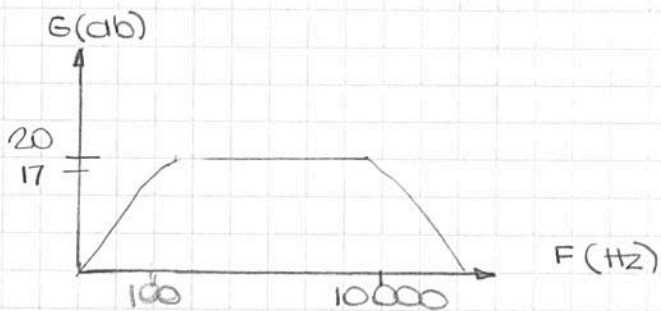

⑥ $G_v = 1 = 20 \log_{10}(1) = 0$

$f_{inf} = 10$

$f_{sup} = 100000$

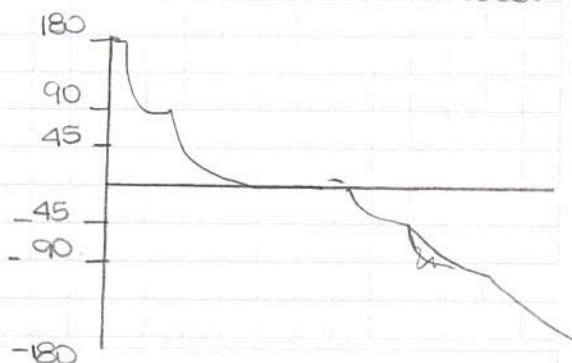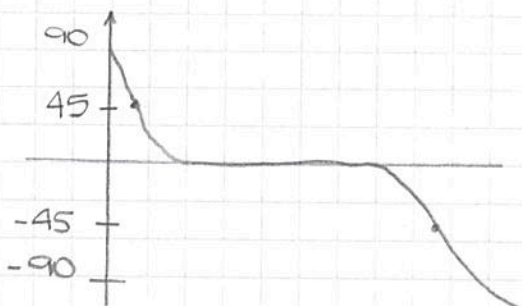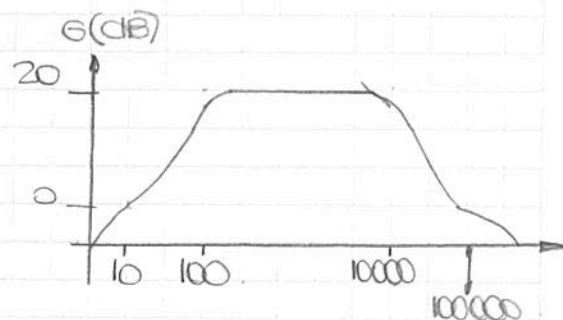

IDEALES:
 HIPOTESIS
 $\checkmark G = \infty$
 $\checkmark R_i = \infty$
 $\checkmark R_o = 0$


1) A) No inverting

$$G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2} = \frac{470 + 2,2}{2,2} = 214,63$$

B) Inverting


$$G = \frac{V_o}{V_i} = -\frac{R_1}{R_2} = -\frac{330}{10} = -33$$

2)

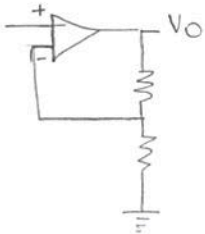

$$G = 100 = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$$

3)

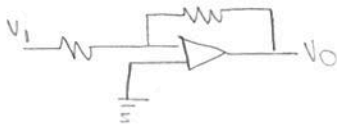


$$G = -50$$

Repetición señales
 Buffer?

4)

5)

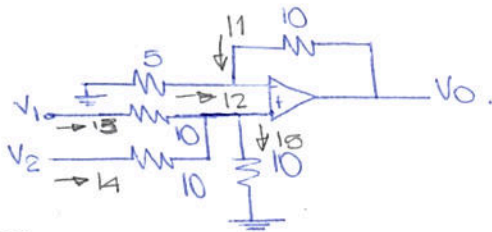

V-

$$I_1 = -I_2$$

$$(0 - V_-) = I_2 \cdot 5 \rightarrow I_2 = -V_- / 5$$

$$(V_o - V_-) = I_1 \cdot 10 = -I_2 \cdot 10 \rightarrow I_2 = \frac{V_- - V_o}{10}$$

$$\left\{ \begin{aligned} -\frac{V_-}{5} &= \frac{V_- - V_o}{10} \end{aligned} \right.$$

$$\frac{V_-}{10} + \frac{V_-}{5} = \frac{V_o}{10}$$

$$\frac{V_-}{10} + \frac{2V_-}{10} = \frac{V_o}{10}$$

$$\frac{3V_-}{10} = \frac{V_o}{10} \Rightarrow \boxed{V_- = \frac{V_o}{3}}$$

$$V_o = 3V_-$$

$$13 + 14 = 15$$

$$\textcircled{V_+} (V_1 - V_+) = 13 \cdot 10 \rightarrow 13 = (V_1 - V_+) / 10$$

$$(V_2 - V_+) = 14 \cdot 10 \rightarrow 14 = (V_2 - V_+) / 10$$

$$(V_+ - 0) = 15 \cdot 10 = (13 + 14) \cdot 10$$

$$V_+ = \left[\frac{(V_1 - V_+)}{10} + \frac{(V_2 - V_+)}{10} \right] \times 10 = V_1 - V_+ + V_2 - V_+ = V_1 + V_2 - 2V_+$$

$$3V_+ = V_1 + V_2$$


$$V_+ = V_-$$

$$\boxed{V_+ = \frac{V_1 + V_2}{3}}$$

$$V_o = 3V_- = 3V_+ = \frac{3(V_1 + V_2)}{3} = V_1 + V_2$$

6

RESTADOR

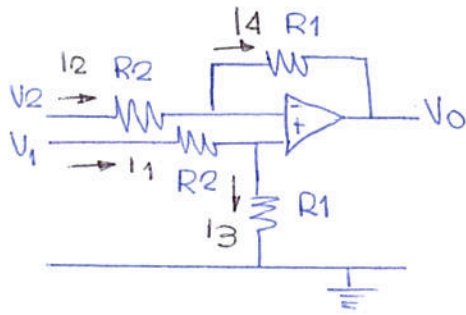

$$V_0 = 10 (V_1 - V_2)$$

$$(1) (V_1 - V_+) = I_1 R_2$$

$$(2) (V_2 - V_-) = I_2 R_2$$

$$(3) V_+ = I_3 R_1$$

$$(4) (V_- - V_0) = I_4 R_1$$

$$I_1 = I_3$$

$$\frac{V_1 - V_+}{R_2} = \frac{V_+}{R_1}$$

$$\frac{V_1 - V_+}{R_2} = \frac{V_+}{R_1}$$

$$\frac{1}{R_2} (V_1 - V_+) = \frac{V_+}{R_1}$$

$$V_1 - V_+ = V_+ \frac{R_2}{R_1}$$

$$V_+ \left(1 + \frac{R_2}{R_1}\right) = V_1$$

$$V_+ = V_1 \cdot \frac{R_1}{R_1 + R_2}$$

$$I_2 = I_4$$

$$\frac{V_2 - V_-}{R_2} = \frac{V_- - V_0}{R_1}$$

$$V_2 - V_- = \frac{R_2}{R_1} (V_- - V_0)$$

$$\frac{R_2}{R_1} V_0 = \frac{R_2}{R_1} V_- - V_2 + V_-$$

$$\frac{R_2}{R_1} V_0 = \left(\frac{R_2}{R_1} + 1\right) V_- - V_2$$


$$\frac{R_2}{R_1} V_0 = \frac{R_2 + R_1}{R_1} V_- - V_2$$

$$V_0 = \frac{R_1}{R_2} \left(\frac{R_2 + R_1}{R_1}\right) V_- - V_2 \frac{R_1}{R_2}$$

$$\Rightarrow V_0 = \frac{R_2 + R_1}{R_2} \cdot \frac{R_1}{R_1 + R_2} \cdot V_1 - V_2 \frac{R_1}{R_2} = \boxed{(V_1 - V_2) \frac{R_1}{R_2}}$$

$$\frac{R_1}{R_2} = 10 \left\{ \begin{array}{l} R_1 = 10 \mu\Omega \\ R_2 = 1 \mu\Omega \end{array} \right.$$

7 SUMADOR INVERSOR

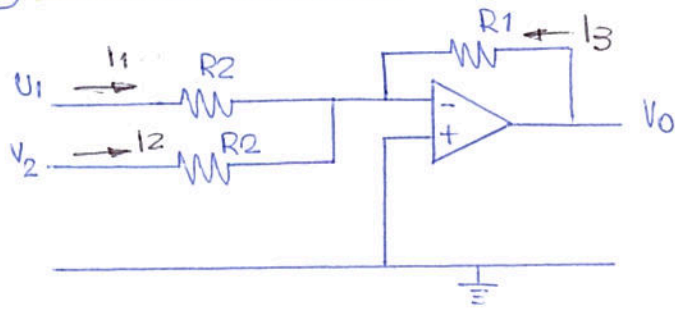

(1) $I_1 + I_2 = -I_3$

(2) $V_1 = I_1 R_2$

(3) $V_2 = I_2 R_2$


(4) $V_0 = I_3 R_1 = (-I_1 - I_2) R_1$

$$V_0 = \left(-\frac{V_1}{R_2} - \frac{V_2}{R_2} \right) R_1$$

$$V_0 = - (V_1 + V_2) \frac{R_1}{R_2}$$

$R_1 = R_2$


BUFFER DE GANANCIA UNITARIA

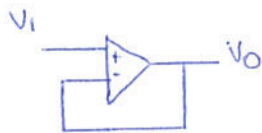

$$G = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + 1 = \frac{0}{\infty} + 1 = 1$$

$R_1 = 0, R_2 = \infty$


CONVERTIDOR CORRIENTE - TENSION

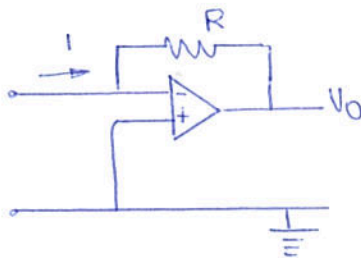

$V_0 = -IR$

AMPLIFICADOR NO-INVERSOR

(entra por el +)

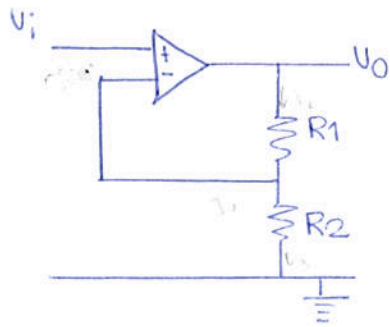


$$V_i = V_+ = V_-$$

$$V_- = V_o \cdot \frac{R_2}{R_1 + R_2} = V_i$$

$$G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$$

AMPLIFICADOR INVERSOR

(entra por el -)

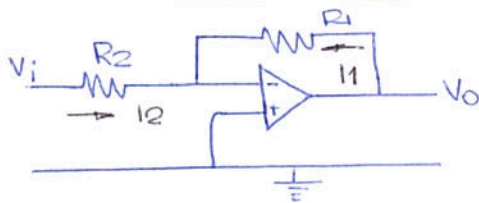


$$V_- = V_+ = 0$$

$$I_1 = -I_2$$

$$I_1 = \frac{V_o}{R_1} \quad I_2 = \frac{V_i}{R_2} \quad \Rightarrow \quad \frac{V_o}{R_1} = -\frac{V_i}{R_2} \quad \Rightarrow \quad G = \frac{V_o}{V_i} = -\frac{R_1}{R_2}$$


TP 6 : ALGEBRA DE BOOLE

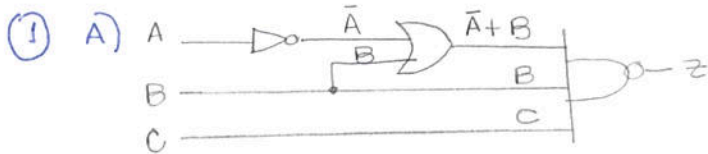

$$\begin{aligned}
 Z &= \overline{(\bar{A}+B)} B C \\
 &= \overline{(\bar{A}+B)} + \bar{B} + \bar{C} \\
 &= \underbrace{A + B}_{\bar{B}} + \bar{B} + \bar{C} = \bar{B} + \bar{C}
 \end{aligned}$$


TABLA DE VERDAD

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

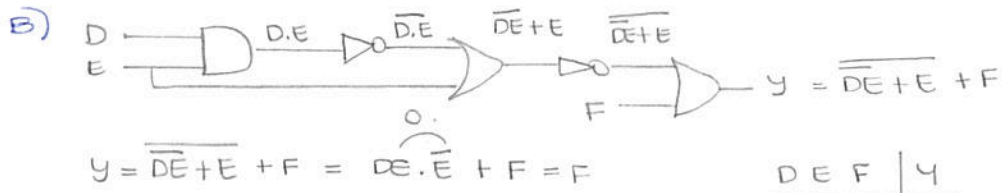

D	E	F	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

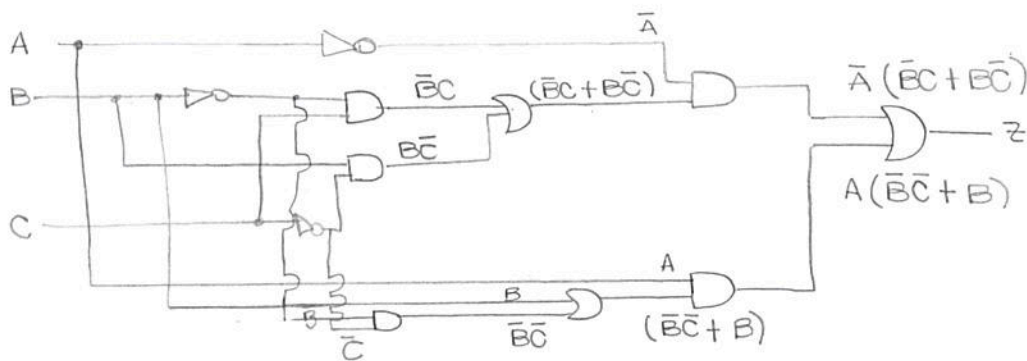② A)
$$\begin{aligned}
 Z &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B\bar{C}) \uparrow 1 \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B(\bar{C} + C)) = \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B)
 \end{aligned}$$



② B)
$$Y = \bar{A}\bar{B}C\bar{D} + \bar{A}BCD + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + AB\bar{C}\bar{D} + AB\bar{C}D + ABCD$$

$$W = \bar{A}\bar{B} + AB(C + \bar{D})$$

$$\begin{aligned}\bar{W} &= \overline{\bar{A}\bar{B} + AB(C + \bar{D})} = AB \cdot \overline{AB(C + \bar{D})} = AB \cdot (\bar{A} + \bar{B} + \overline{C + \bar{D}}) \\ &= AB(\bar{A} + \bar{B} + (\bar{C} \cdot D))\end{aligned}$$

$$(7) \quad A) \quad Y = \overline{\bar{A}BC} \cdot \overline{DB} \cdot \overline{AC\bar{D}} = \bar{A}BC + DB + AC\bar{D} = C(\bar{A}B + A\bar{D}) + DB$$

B)

TP 7: SIMPLIFICACIÓN DE F. BOOLEANAS

1) A) $Z = \bar{A}B + \bar{A}\bar{C} + \bar{A} + AD(\bar{B}\bar{C} + BC) = \bar{A} + AD\bar{B}\bar{C} + ABCD$

A/B	00	01	11	10
00	1	1		
01	1	1		1
11	1	1	1	
10	1	1		

B) $Y = \sum_m (0,2,3,4,5,6,8,9,10,12,13,14,15)$

A/B	00	01	11	10
00	1	1	1	1
01	0	1	1	1
11	1	0	1	0
10	1	1	1	1

$Y = \bar{D} + \bar{A}\bar{C} + AB + B\bar{C} + \bar{A}\bar{B}C$

2)

AB	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	1	1	1	0
10	0	1	0	1

- $\bar{A}\bar{C}\bar{D}$
- $\bar{A}\bar{B}\bar{D}$
- $\bar{B}\bar{C}\bar{D}$
- $\bar{A}\bar{B}\bar{C}$


$Y = \dots + \dots$ Miniterminos

$1 = \bar{A} + \bar{B} + \bar{C} + D$
 $4 = \bar{A} + B + \bar{C} + \bar{D}$
 $2 = \bar{A} + \bar{B} + C + \bar{D}$
 $13 = A + B + \bar{C} + D$
 $14 = A + B + C + \bar{D}$
 $11 = A + \bar{B} + C + D$



Al revés!
los negados
no van mejorados

TP 5

1) B)

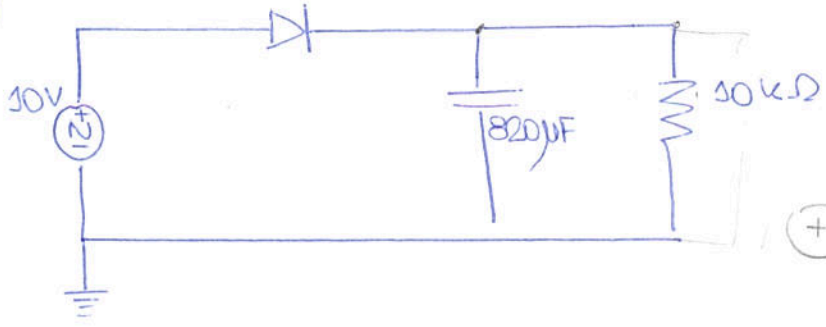


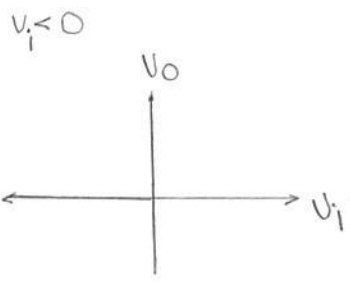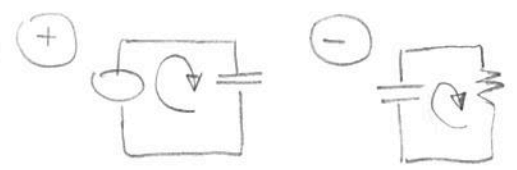Cuando $V_i > 0$ la corriente pasa por el capacitor




Cuando V de la fuente (V_i) es:


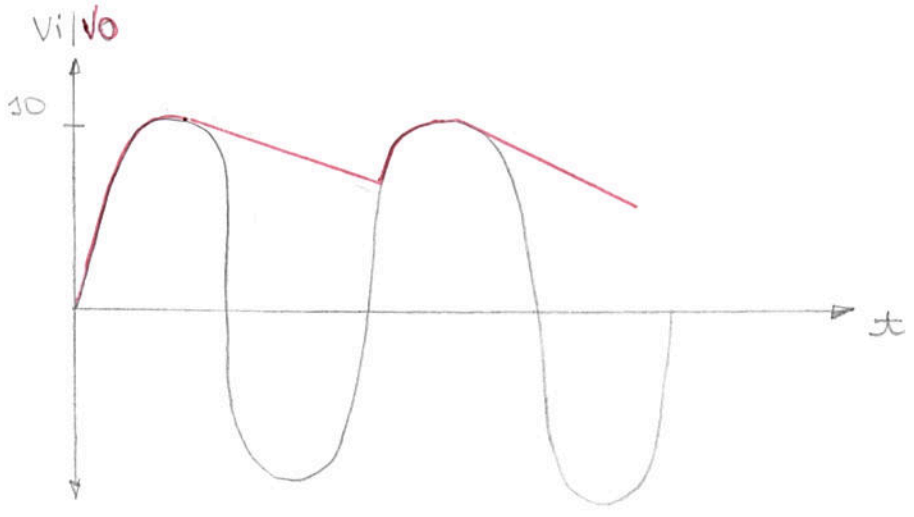
- $>$ al V_{cap} → cap. se carga
- $<$ al V_{cap} → cap. se descarga




A)

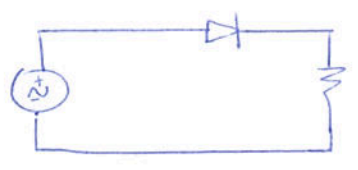

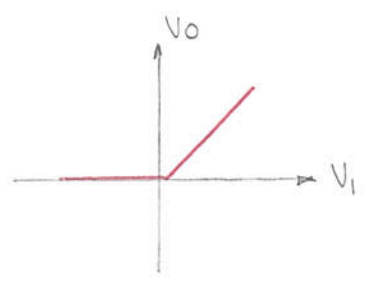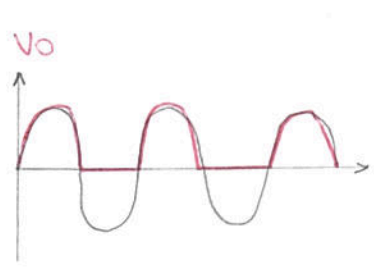$V_i > 0 \quad V_o = V_i$
 $V_i < 0 \quad V_o = 0$




2) i)

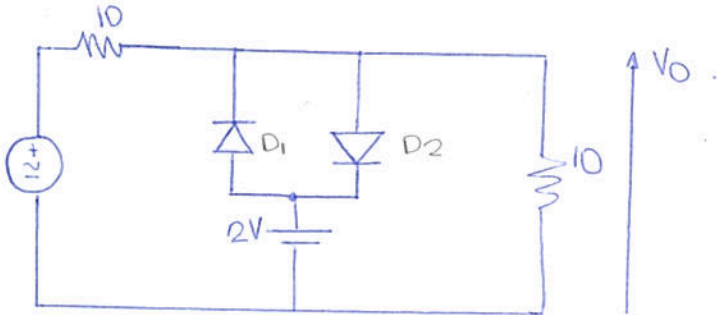


4 casos:

1) D1 inv.
D2 dir.

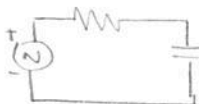


$V_0 = 2V$

2) D1 dir.
D2 inv.




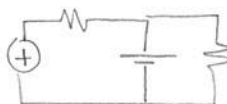


$V_0 = 2V$





3) D1 inv.
D2 inv.

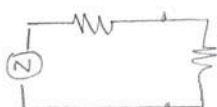

$V_0 = \frac{V_i}{2}$

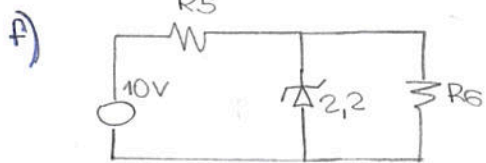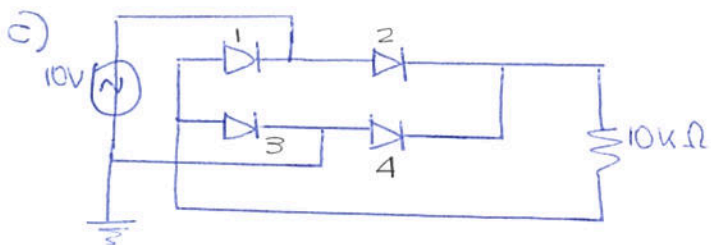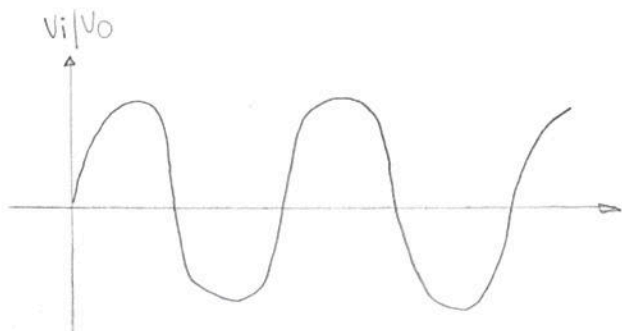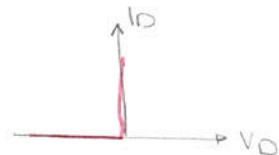

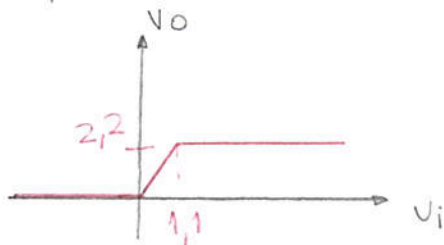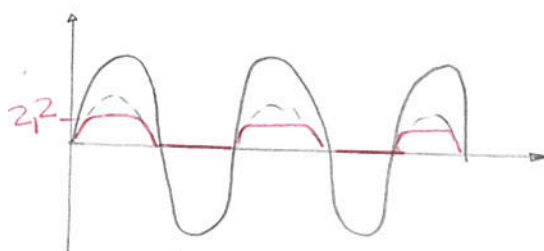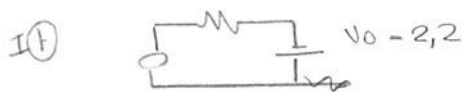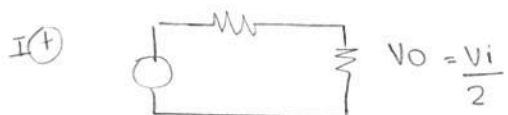corriente \oplus $\rightarrow V_i > 2,2$ (Δ fuente)
 $\rightarrow V_i < 2,2$ (Δ wo paso I)



g)

