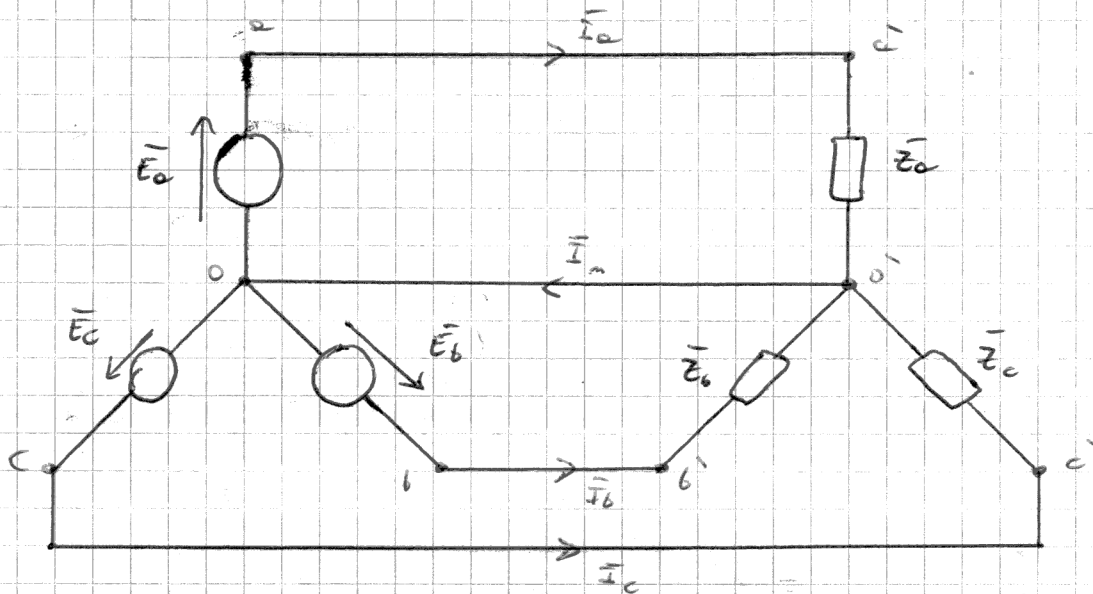


PRÁCTICA 13

POTENCIA EN SISTEMAS TRIFÁSICOS

13.1)



$$\begin{cases} \bar{E}_a = 220 e^{j0^\circ} \text{ V} \\ \bar{E}_b = 220 e^{j240^\circ} \text{ V} \\ \bar{E}_c = 220 e^{j120^\circ} \text{ V} \end{cases}$$

$$\bar{Z}_a = \bar{Z}_b = \bar{Z}_c = 11 e^{j30^\circ} \Omega$$

LVGG:

$$\bar{E}_a = \bar{I}_a \bar{Z}_a \Rightarrow \bar{I}_a = \frac{\bar{E}_a}{\bar{Z}_a}$$

IDEM \bar{I}_b y $\bar{I}_c =$

$$\begin{cases} \bar{I}_a = 20 e^{-j30^\circ} \\ \bar{I}_b = 20 e^{j210^\circ} \\ \bar{I}_c = 20 e^{j90^\circ} \end{cases}$$

ENTONCES:

$$\bar{S}_{2a} = \bar{V}_a \cdot \bar{I}_a^* = 4400 e^{j30^\circ} \text{ VA}$$

$$\bar{S}_{2b} = \bar{V}_b \cdot \bar{I}_b^* = 4400 e^{j30^\circ} \text{ VA}$$

$$\bar{S}_{2c} = \bar{V}_c \cdot \bar{I}_c^* = 4400 e^{j30^\circ} \text{ VA}$$

13.2)

$\bar{Z}_a = \bar{Z}_b$ DE CUYA SOLUCION SON LAS MISMAS DEL PROBLEMA ANTERIOR

LUSGO:

$$\bar{S}_{2a} = \bar{V}_a \cdot \bar{I}_a^* = 4400 e^{j30^\circ} \text{ VA}$$

$$\bar{S}_{2b} = \bar{V}_b \cdot \bar{I}_b^* = 4400 e^{j30^\circ} \text{ VA}$$

Por lo tanto, como $\bar{Z}_c = 55 e^{j30^\circ} \Omega$, la potencia \bar{S}_{2c}


ABSORBIDA SEM =

$$\bar{S}_{2c} = \bar{V}_c \cdot \bar{I}_c^* = 8800 e^{j30^\circ} \text{ VA}$$

LUSGO:

$$\bar{S}_{\text{TOTAL}} = 17600 e^{j30^\circ} \text{ VA}$$

13.5)

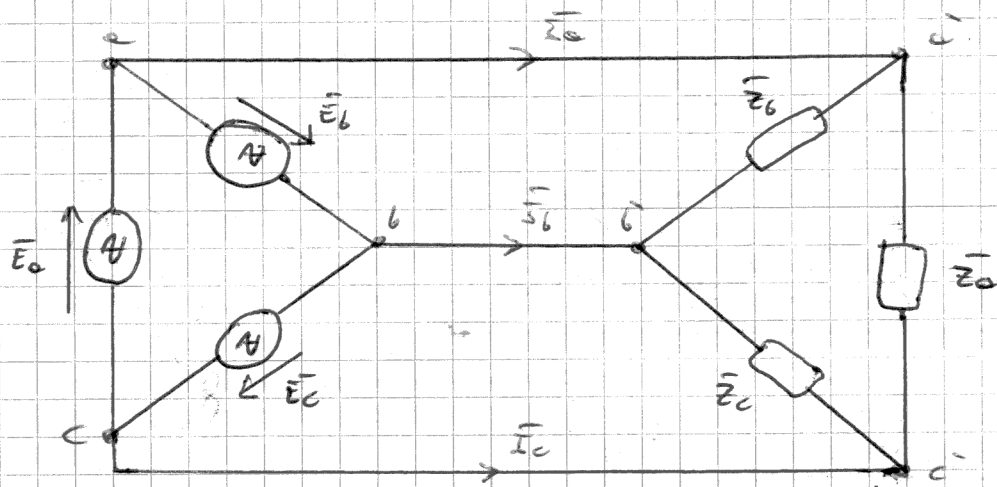

$$\begin{cases} \bar{E}_a = 220 \text{ V } e^{j0^\circ} \\ \bar{E}_b = 220 \text{ V } e^{j240^\circ} \\ \bar{E}_c = 220 \text{ V } e^{j120^\circ} \end{cases} \quad \bar{Z}_a = \bar{Z}_b = \bar{Z}_c = 11 e^{j30^\circ} \Omega$$

ENTONCES:

$$\bar{E}_a = \bar{I}'_{ac} \cdot \bar{Z}_a \Rightarrow \bar{I}'_{ac} = 20 e^{-j30^\circ} = \bar{I}_{ca}$$

$$\bar{E}_b = \bar{I}'_{bc} \cdot \bar{Z}_b \Rightarrow \bar{I}'_{bc} = 20 e^{j210^\circ} = \bar{I}_{cb}$$

$$\bar{E}_c = \bar{I}'_{cb} \cdot \bar{Z}_c \Rightarrow \bar{I}'_{cb} = 20 e^{j90^\circ} = \bar{I}_{bc}$$

Como se observaron las mismas corrientes en el problema

13.1), se puede concluir que las potencias complejas

son las mismas.

$$13.6) \quad \bar{S} = 3 \cdot \bar{V}_{\text{FASE}} \cdot \bar{I}_{\text{FASE}}^*$$

$$\bar{S} = 3 \cdot \frac{V_{\text{LINE}}}{\sqrt{3}} \cdot \bar{I}_{\text{LINE}}^*$$

$$\boxed{\bar{S} = \sqrt{3} \bar{V}_{\text{LINE}} \cdot \bar{I}_{\text{LINE}}^*}$$


PARA CONEXIÓN ESTRELA:

$$\begin{cases} \bar{I}_{\text{FASE}} = \bar{I}_{\text{LINE}} \\ \bar{V}_{\text{LINE}} = \sqrt{3} \bar{V}_{\text{FASE}} \end{cases}$$

PARA CONEXIÓN TRIÁNGULO:

$$\begin{cases} \bar{I}_{\text{LINE}} = \sqrt{3} \bar{I}_{\text{FASE}} \\ \bar{V}_{\text{LINE}} = \bar{V}_{\text{FASE}} \end{cases}$$

13.7)

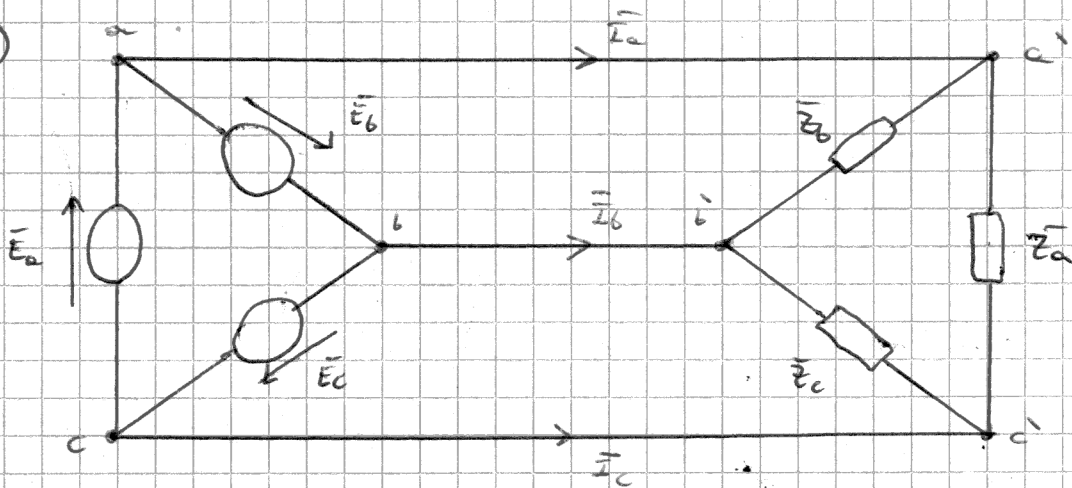

$$\begin{cases} \bar{E}_a = 220 e^{j0^\circ} \text{ V} \\ \bar{E}_b = 220 e^{j240^\circ} \text{ V} \\ \bar{E}_c = 220 e^{j120^\circ} \text{ V} \end{cases}$$

$$\begin{cases} \bar{Z}_a = 2,6 e^{j16^\circ} \text{ } \Omega \\ \bar{Z}_b = 9 e^{j36^\circ} \text{ } \Omega \\ \bar{Z}_c = 20 e^{j0^\circ} \text{ } \Omega \end{cases}$$

Los voltajes

$$\bar{E}_a = \bar{V}_a = \bar{I}'_{ca} \cdot \bar{Z}_a \Rightarrow$$

$$\bar{I}'_{ca} = 84,62 e^{-j16^\circ} \text{ A}$$

$$\bar{E}_b = \bar{V}_b = \bar{I}'_{bc} \cdot \bar{Z}_b \Rightarrow$$

$$\bar{I}'_{bc} = 24,44 e^{j24^\circ} \text{ A}$$

$$\bar{E}_c = \bar{V}_c = \bar{I}'_{cb} \cdot \bar{Z}_c \Rightarrow$$

$$\bar{I}'_{cb} = 11 e^{j120^\circ} \text{ A}$$

Los potencias absorbidas son:

$$\bar{S}_{Za} = \bar{V}_a \cdot \bar{I}'_{ca}^* = 18616,4 e^{j16^\circ} \text{ VA}$$

$$\bar{S}_{Zb} = \bar{V}_b \cdot \bar{I}'_{bc}^* = 5376,8 e^{j36^\circ} \text{ VA}$$

$$\bar{S}_{Zc} = \bar{V}_c \cdot \bar{I}'_{cb}^* = 2420 e^{j0^\circ} \text{ VA}$$

LV600, 50 T1622 216 =

$$P = 24 \text{ kGS}, 15 \text{ W}$$


$$Q = 8271, 279 \text{ VA}$$

Y R FACTOR 23 1070ds 65 =

$$\cos \varphi = 0,9478$$

$$\varphi = 18,58^\circ$$

13.11)

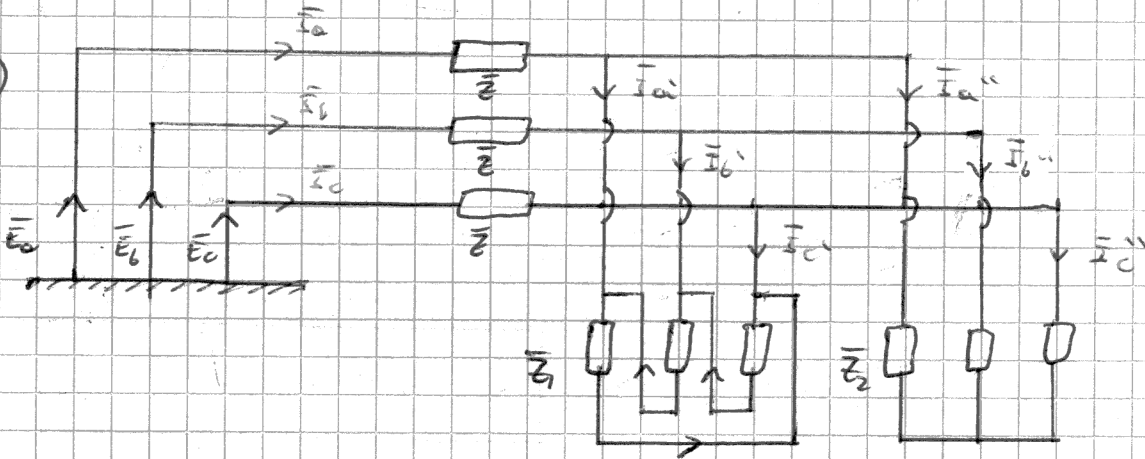

$$\begin{cases} \bar{Z} = 4,23 e^{j82,87^\circ} \Omega \\ \bar{Z}_1 = 220,77 e^{j14^\circ} \Omega \\ \bar{Z}_2 = 40 e^{j0^\circ} \Omega \end{cases}$$

$$\begin{cases} \bar{E}_0 = 750 e^{j0^\circ} \text{ V} \\ \bar{E}_6 = 750 e^{j240^\circ} \text{ V} \\ \bar{E}_c = 750 e^{j120^\circ} \text{ V} \end{cases}$$

$$\bar{E}_a - \bar{I}_a \cdot \bar{Z} - \bar{I}_a'' \cdot \bar{Z}_2 = 0$$

$$\bar{E}_a - \bar{I}_a \bar{Z} - \bar{I}_{a'c} \bar{Z}_1 + \bar{I}_c \bar{Z} - \bar{E}_b = 0$$

$$\bar{I}_a = \bar{I}_{a'} + \bar{I}_{a''}$$

Además:

$$\bar{I}_{a'c} = \bar{I}_{a'} + \bar{I}_{b'a}$$

$$\bar{I}_{b'a} = \bar{I}_{b'} + \bar{I}_{c'a}$$

$$\bar{I}_{c'a} = \bar{I}_{c'} + \bar{I}_{a'c}$$

Y:

$$\bar{I}_{a'} + \bar{I}_{b'} + \bar{I}_{c'} = 0$$

$$\bar{I}_{a''} + \bar{I}_{b''} + \bar{I}_{c''} = 0$$

Usando:

$$\bar{I}_c = \bar{I}_a \cdot e^{j120^\circ}$$

$$\bar{I}_{c'} = \bar{I}_{a'} \cdot e^{j120^\circ}$$

$$\bar{I}_{b'c''} = \bar{I}_{a''} \cdot e^{j120^\circ}$$

LUSGS =

$$\bar{I}_{a0} (1 - e^{j240^\circ}) = \bar{I}_{a1}$$

ENTOROS =

$$\bar{E}_a - \bar{I}_a \bar{Z} - \frac{\bar{I}_{a1}}{(1 - e^{j240^\circ})} \bar{Z}_1 + \bar{I}_a e^{j120^\circ} \bar{Z} - \bar{E}_b = 0$$

$$\bar{E}_a - \bar{I}_a \bar{Z} - \bar{I}_{a1} \bar{Z}_2 = 0$$

$$\bar{E}_b - \bar{I}_{a1} \bar{Z} - \bar{I}_{a1} (-\bar{Z} - \bar{Z}_2) = 0$$


$$\bar{I}_{a1} = \frac{\bar{E}_a - \bar{I}_{a1} \bar{Z}}{-\bar{Z} - \bar{Z}_2}$$

$$\bar{E}_b - \bar{I}_{a1} \bar{Z} - \left(\frac{\bar{E}_a - \bar{I}_{a1} \bar{Z}}{-\bar{Z} - \bar{Z}_2} \right) \bar{Z} - \frac{\bar{I}_{a1} \bar{Z}_1}{(1.5 + 0.866j)}$$

$$+ \bar{I}_{a1} e^{j120^\circ} \bar{Z} + \left(\frac{\bar{E}_a - \bar{I}_{a1} \bar{Z}}{-\bar{Z} - \bar{Z}_2} \right) e^{j120^\circ} \bar{Z}$$

$$- \bar{E}_b = 0$$

13.15)

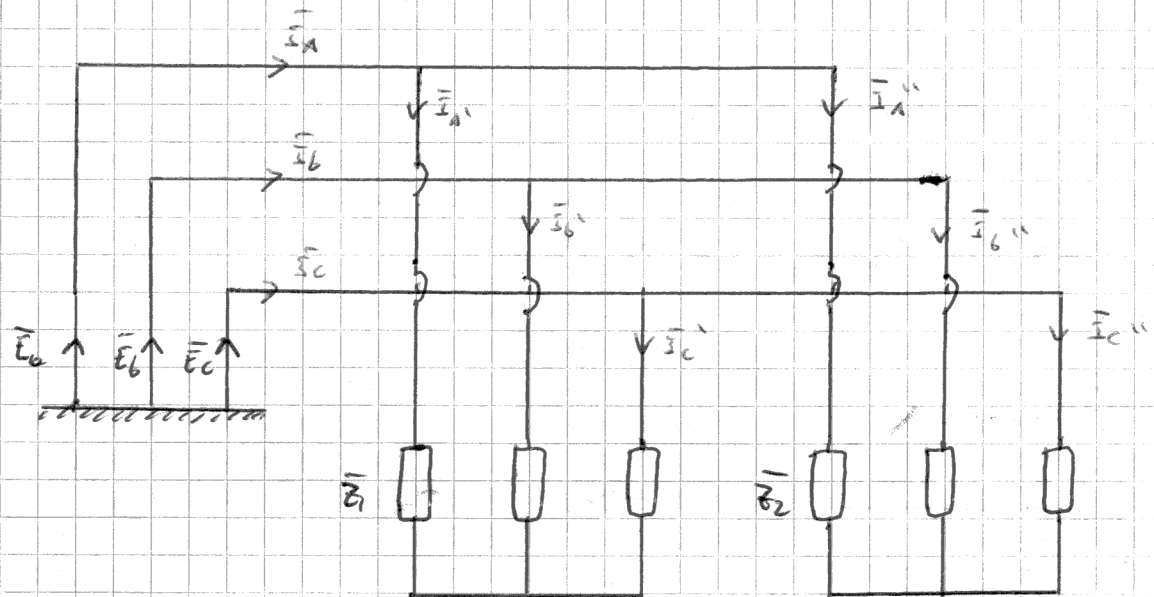

$S = 100 \text{ KVA}$

TE- \sin 240 V

$E_a = 240 e^{j0^\circ} \text{ V}$

$\Rightarrow \cos \theta = 0,8 \Rightarrow \theta = 36,87^\circ$

$P_{21} = 65 \text{ KW}$

$\bar{S} = 100 \angle 36,87^\circ \text{ KVA}$

LU862 =

$\bar{S}_{total} - \bar{P}_{21} = \bar{P}_{22} = (80 + 60j) \text{ KVA} - 65 \text{ KVA}$

$\bar{P}_{22} = (15 + j 60) \text{ KVA} = 61,8 e^{j 76,1^\circ} \text{ KVA}$

Leistungen:

$$\begin{cases} \bar{P}_{22} = 20,6 e^{j 70,1^\circ} \text{ kVA} \\ \bar{P}_{21} = 21,66 \text{ kW} \end{cases}$$

$$\Rightarrow \bar{S}' = 33,33 e^{j 30,57^\circ} \text{ kVA}$$

Admittanz:

$$\bar{S}_{22} = \frac{\bar{V}_0^2}{\bar{Z}_2^*} \Rightarrow \bar{S}_{21} \bar{Z}_2^* = \frac{\bar{V}_0^2}{\bar{S}_{22}}$$

Erwartung:

$$\bar{Z}_2^* = \frac{57600 \text{ V}^2}{20660 e^{j 70,1^\circ} \text{ VA}}$$

$$\bar{Z}_2^* = 2,79 e^{j(-70,1^\circ)} \Omega$$

Ergebnis:

$$\bar{Z}_2 = 2,79 e^{j 70,1^\circ} \Omega$$