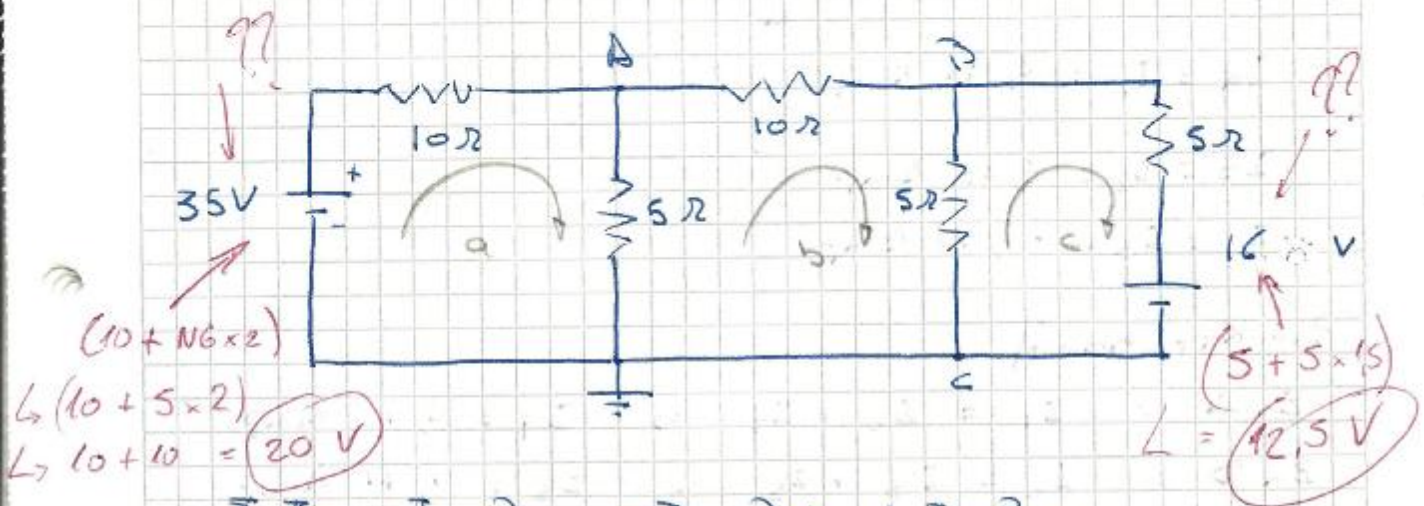


Ejercicio n° 1

Resolver por método de las mallas



$$\sum E_a = I_a \cdot R_{aa} + I_b \cdot R_{ab} + I_c \cdot R_{ac}$$

$$\sum E_b = I_a \cdot R_{ab} + I_b \cdot R_{bb} + I_c \cdot R_{bc}$$

$$\sum E_c = I_a \cdot R_{ac} + I_b \cdot R_{bc} + I_c \cdot R_{cc}$$

$$35 = I_a (10 + 5) + I_b (-5) + I_c \cdot 0$$

$$0 = I_a (-5) + I_b (20) + I_c (-5)$$

$$-16 = I_a \cdot 0 + I_b (-5) + I_c (10)$$


$$\begin{array}{c|ccc|c} 35 & 15 & -5 & 0 & I_a \\ 0 & -5 & 20 & -5 & I_b \\ -16 & 0 & -5 & 10 & I_c \end{array}$$

$$I_a = 2,41$$

$$\Rightarrow I_b = 0,23$$

$$I_c = -1,48$$

↳ sentido opuesto al tomado

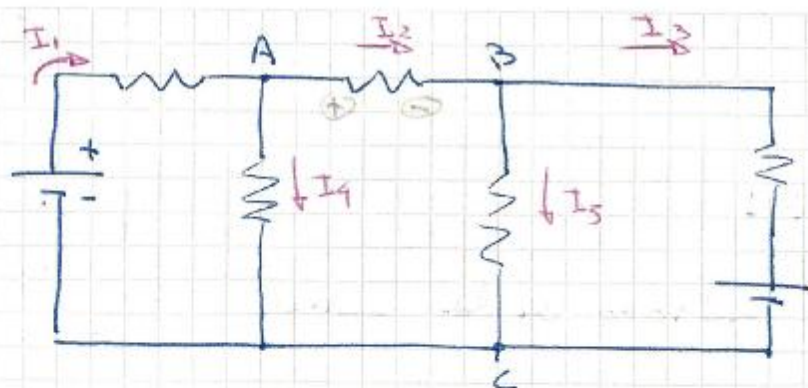

$$I_a = I_1 = 2,41 \text{ Amp}$$

$$I_b = I_2 = 0,23 \text{ Amp}$$

$$I_c = I_3 = -1,48 \text{ Amp}$$

Por Kirchhoff

$$\text{En A : } I_1 = I_2 + I_4 \Rightarrow I_4 = 2,18 \text{ Amp}$$

$$\text{En B : } I_2 = I_3 + I_5 \Rightarrow I_5 = 1,71 \text{ Amp}$$



• Cálculo de tensión entre los nodos A y B

$$U_{A-B} = -I_2 \cdot R = -(0,23 \text{ A} \cdot 10 \Omega)$$

$$U_{A-B} = -2,3 \text{ V} \quad \checkmark$$


Ejercicio n° 2

Resolver por Thévenin

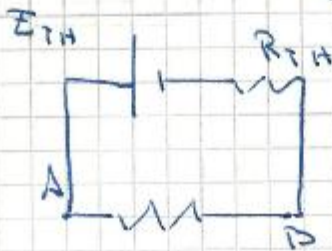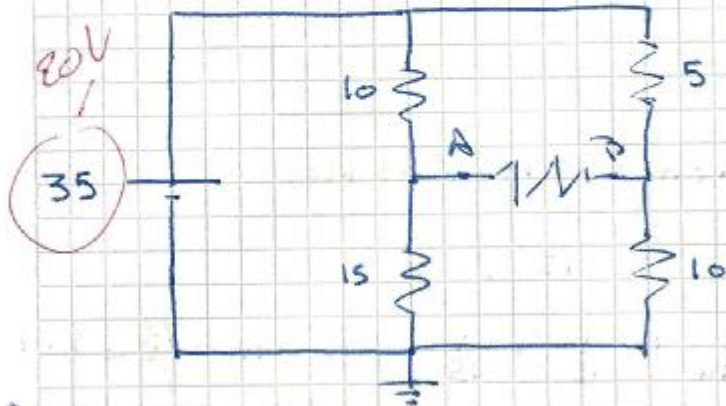

$E_{TH} = (V_A - V_B)$

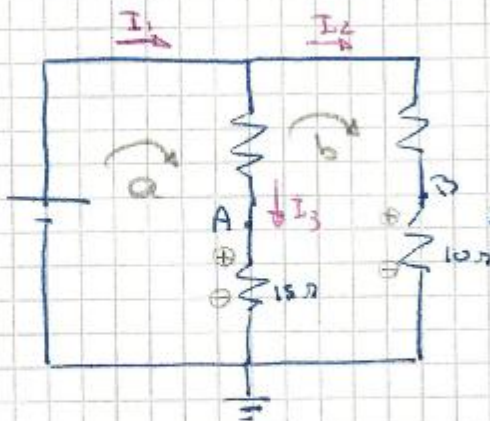obtenemos las corrientes del circuito Resto



Por mallas

$\sum Z_a = I_a \cdot R_{aa} + I_b \cdot R_{ab}$

$\sum Z_b = I_a \cdot R_{ab} + I_b \cdot R_{bb}$

$35 = I_a \cdot 25 + I_b \cdot -25$

$0 = I_a \cdot -25 + I_b \cdot 40$

$$\begin{bmatrix} 35 \\ 0 \end{bmatrix} = \begin{bmatrix} 25 & -25 \\ -25 & 40 \end{bmatrix} \cdot \begin{bmatrix} I_a \\ I_b \end{bmatrix} \Rightarrow$$

$I_a = 3,73 \text{ Amp} = I_1$

$I_b = 2,33 \text{ Amp} = I_2$


$I_1 = I_2 + I_3$

\Rightarrow

$1,43 \text{ Amp} = I_3$

$$\begin{aligned}
 E_{TH} &= (V_D - V_D) = + I_2 \cdot 10\Omega - I_3 \cdot 15\Omega \\
 &= 3,33 \cdot 10 - 1,43 \cdot 15 \\
 &= \underline{\underline{1,85 \text{ V}}} \quad \checkmark
 \end{aligned}$$


• Calculamos la R_{TH}

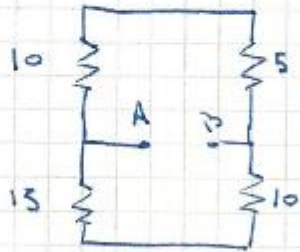

$$R_{TH} = (10 + 5) \parallel (15 + 10) \quad \checkmark$$

$$= 15 \parallel 25 \quad \checkmark$$


$$\frac{1}{R_{TH}} = \frac{1}{15} + \frac{1}{25} \Rightarrow R_{TH} = \frac{75}{8} = \underline{\underline{9,375 \Omega}} \quad \checkmark$$

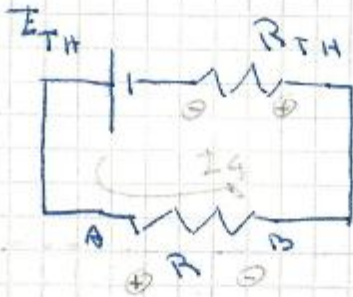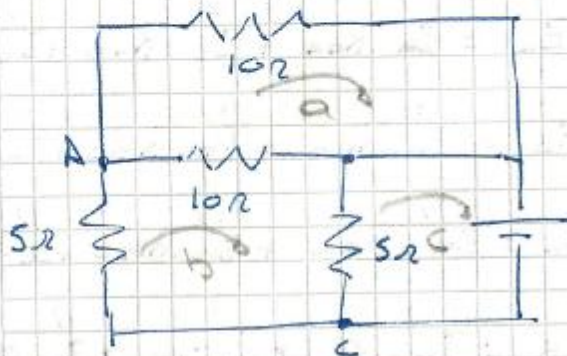

Ejercicio 3

Resolverse por el teorema de la superposición

Estado 1

Por mallas

$$\sum E_a = I_a' \cdot R_{aa} + I_b' \cdot R_{ab} + I_c' \cdot R_{ac}$$

$$\sum E_b = I_a' \cdot R_{ba} + I_b' \cdot R_{bb} + I_c' \cdot R_{bc}$$

$$\sum E_c = I_a' \cdot R_{ca} + I_b' \cdot R_{cb} + I_c' \cdot R_{cc}$$

$$0 = I_a' \cdot 20 + I_b' \cdot -10 + I_c' \cdot 0$$

$$0 = I_a' \cdot -10 + I_b' \cdot 20 + I_c' \cdot -5$$

$$-16 = I_a' \cdot 0 + I_b' \cdot -5 + I_c' \cdot 5$$


$$I_a' = -8$$

$$I_b' = -1,6$$

$$I_c' = -4,8$$


$$\begin{vmatrix} 0 \\ 0 \\ -16 \end{vmatrix} = \begin{vmatrix} 20 & -10 & 0 \\ -10 & 20 & -5 \\ 0 & -5 & 5 \end{vmatrix} \cdot \begin{vmatrix} I_a' \\ I_b' \\ I_c' \end{vmatrix}$$

Nos queda

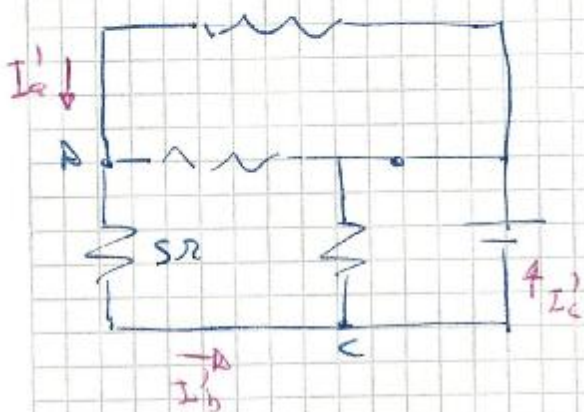

Resolver por el teorema de la superposición

Estado 2

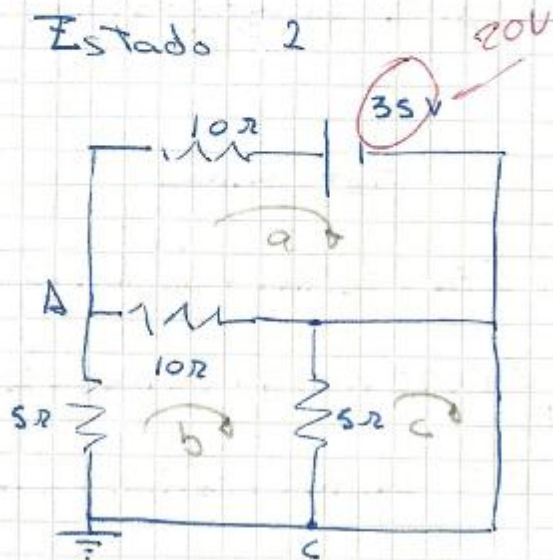

Por mallas

$$\sum E_a = I_a'' \cdot R_{aa} + I_b'' \cdot R_{ab} + I_c'' \cdot R_{ac}$$

$$\sum E_b = I_a'' \cdot R_{ba} + I_b'' \cdot R_{bb} + I_c'' \cdot R_{bc}$$

$$\sum E_c = I_a'' \cdot R_{ca} + I_b'' \cdot R_{cb} + I_c'' \cdot R_{cc}$$

$$-35 = I_a'' \cdot 20 + I_b'' \cdot 10 + I_c'' \cdot 0$$

$$0 = I_a'' \cdot -10 + I_b'' \cdot 20 + I_c'' \cdot -5$$

$$0 = I_a'' \cdot 0 + I_b'' \cdot -5 + I_c'' \cdot 5$$

$$I_a'' = -2,62$$


$$I_b'' = -1,75$$

$$I_c'' = -1,75$$

$$\begin{vmatrix} -35 \\ 0 \\ 0 \end{vmatrix} = \begin{vmatrix} 20 & -10 & 0 \\ -10 & 20 & -5 \\ 0 & -5 & 5 \end{vmatrix} \begin{vmatrix} I_a'' \\ I_b'' \\ I_c'' \end{vmatrix}$$

↑ sentido opuesto al dibujado anteriormente

Nos queda:

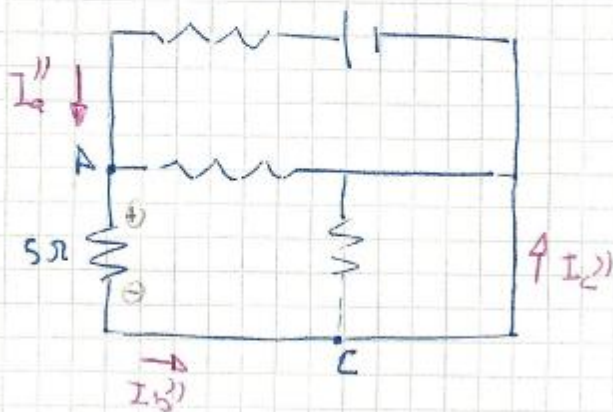

$$I_a' + I_a'' = I_a$$

$$I_b' + I_b'' = I_b \Rightarrow 1,6 + 1,75 = I_b = 3,35 \text{ A}$$

$$I_c' + I_c'' = I_c$$

La caída de tensión entre los nodos D y C

$$V_D - V_C = -3,35 \text{ A} \cdot 5 \Omega = \underline{\underline{-16,75 \text{ Vol.}}}$$